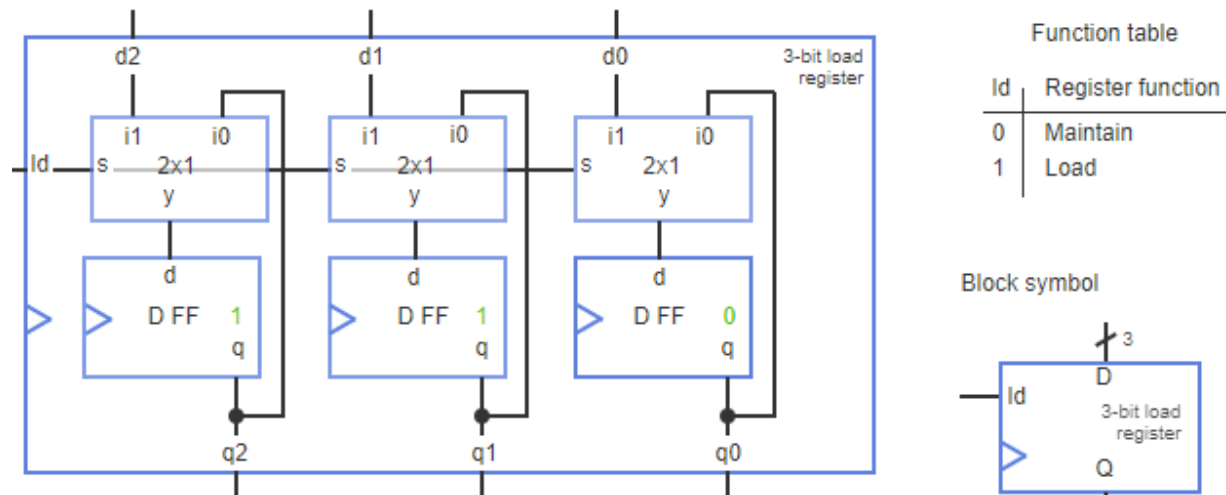


Problem 1) Develop an 8-bit load register similar to the register shown in the diagram below (except yours will be 8-bits wide instead of 3):



Use SW[7:0] for the data input, SW[9] for the Load signal, and Key 1 for the clock signal.

Problem 2) Extend the register in problem 1 to include the functions in the following table:

SW[9:8]	Register Function
00	Maintain (No change in Q)
01	Load (Q = D)
10	Synchronous Clear (Q = 0)
11	Complement (Q = NOT Q)